

IIT JODHPUR
FORMAL VERIFICATION (EEL7770) MINOR-1


Full marks: 15, Time Limit: 1 Hour

Instructions:

1. Answers should be brief and to the point. Unnecessary/Unrelated explanations in the answers should be avoided.
2. You are advised to adopt mathematical reasoning and symbols in all your answers, as far as possible. In case of any kinds of doubt/confusion, kindly take valid assumptions and answer the questions.
3. This exam is OPEN-BOOK. However, it is strongly advised to NOT waste time by looking up to the reference materials for every question.

Q1. [2] Z. Kohavi (a famed scientist on automata theory) gave the below theorem that is known by his name now (Kohavi's Theorem): **Two states of a given FSM with n states are equivalent if and only if they (i.e., those 2 states) are $(n-1)$ -equivalent.** Prove this theorem with any method.

 Q2. [2 + 1] We want to implement the following gate level netlist:



Suppose the RTL designer wrote the following code to implement the above structure:


```
module Example_1 ( q2 ,d ,clk ,rst_n);
output q2 ;
input d , clk,rst_n;
reg q2 ,q1;

always @( posedge clk or negedge rst_n )
if ( ! rst_n ) q1 <= 1'b0 ;
else
begin
q1 <= d ;
q2 <= q1 ;
end
endmodule
```

Is the above RTL equivalent to the designers intention (i.e. the netlist portion shown above)? If your answer is NO, what would be the correct RTL code?


Q3. [3] Provide a formal representation/implementation of a half-adder (1-bit) and full-adder (1-bit) design?

 Q4. [2] Consider the following case of 2 design implementations:




What will be the result when you perform sequential equivalence checking (SEC) on the above designs? Justify your answer.

 
Q5. [3] With any formal method, prove that the below state transition graph represents a modulo-3 counter. (i.e., it counts 3 distinct states, 0, 1, 2) ?



 Q6. [2] Retiming is a popular concept in VLSI design flow to increase the operating frequency of the design. Primarily this technique involves shifting locations of the flip-flops to adjust the delays of the combinational paths in the circuit. Argue in a formal way that the following two designs (first-before retiming, second-after retiming) are equivalent? [+ means an adder block, X means a multiplier block].



Before retiming

 

After retiming